


## Tutorial for Chapter 9 - MSI

→ 9-1. Refer to Figure 9-3. Determine the levels at each decoder output for the following sets of input conditions.

- (a) All inputs LOW
- (b) All inputs LOW except  $E_3 = \text{HIGH}$
- (c) All inputs HIGH except  $\bar{E}_1 = \bar{E}_2 = \text{LOW}$
- (d) All inputs HIGH
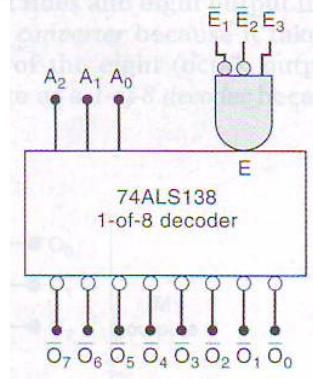
### CHAPTER 9

→ 9-1. (a) All HIGH (b)  $\bar{O}_0 = \text{LOW}$  (c)  $\bar{O}_7 = \text{LOW}$   
(d) All HIGH



→ 9-2. What is the number of inputs and outputs of a decoder that accepts 64 different input combinations?

→ 9-2. Six inputs, 64 outputs  
→ 9-3. (a)  $E_3E_2E_1 = 100$ ;  $[A] =$


→ 9-3. For a 74ALS138, what input conditions will produce the following outputs:

- (a) LOW at  $\bar{O}_6$
- (b) LOW at  $\bar{O}_3$
- (c) LOW at  $\bar{O}_5$
- (d) LOW at  $\bar{O}_0$  and  $\bar{O}_7$ , simultaneously

→ 9-3. (a)  $E_3E_2E_1 = 100$ ;  $[A] = 110$  (b)  $E_3E_2E_1 = 100$ ,  
 $[A] = 011$  (c)  $E_3E_2E_1 = 100$ ;  $[A] = 101$  (d) No input conditions

→ 9-7. The 7442 decoder of Figure 9-5 does not have an ENABLE input. However, we can operate it as a 1-of-8 decoder by not using outputs  $\bar{O}_8$  and  $\bar{O}_9$  and by using the  $D$  input as an ENABLE. This is illustrated in Figure 9-71. Describe how this arrangement works as an enabled 1-of-8 decoder, and state how the level on  $D$  either enables or disables the outputs.

→ 9-7. Enabled when  $D = 0$

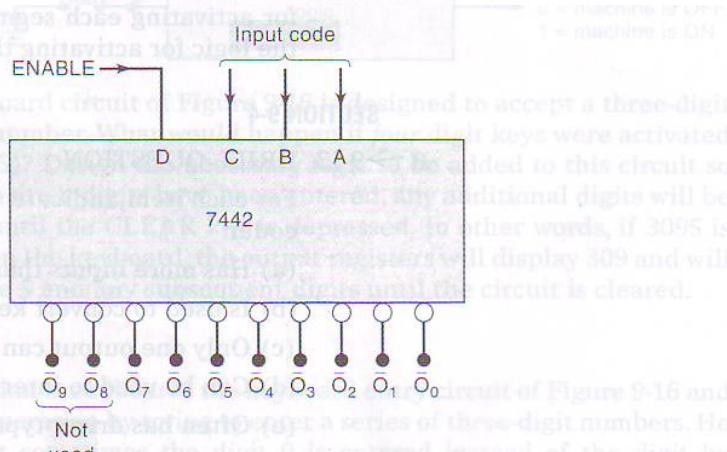

### →9-13. DRILL QUESTION


For each item, indicate whether it is referring to a decoder or an encoder.

- (a) Has more inputs than outputs.
- (b) Is used to convert key actuations to a binary code.
- (c) Only one output can be activated at one time.
- (d) Can be used to interface a BCD input to an LED display.
- (e) Often has driver-type outputs to handle large  $I$  and  $V$ .

→9-13. (a), (b) Encoder (c), (d), (e) Decoder

### →9-14. Determine the output levels for the 74147 encoder when $\bar{A}_8 = \bar{A}_4 = 0$ and all other inputs are HIGH.


→9-14. 0111  
9-17 The fr

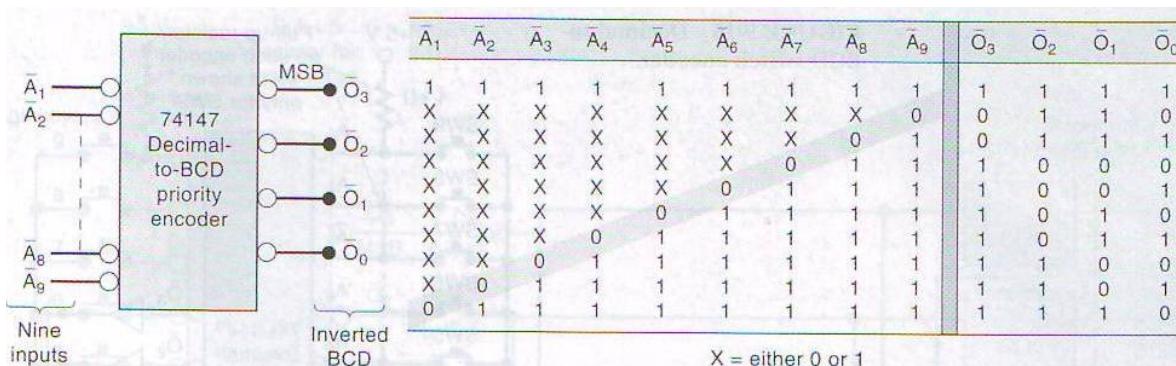

CLOCK.

- 9-29. The circuit in Figure 9-75 uses three two-input multiplexers (Figure 9-19). Determine the function performed by this circuit.

FIGURE 9-75 Problem 9-29.

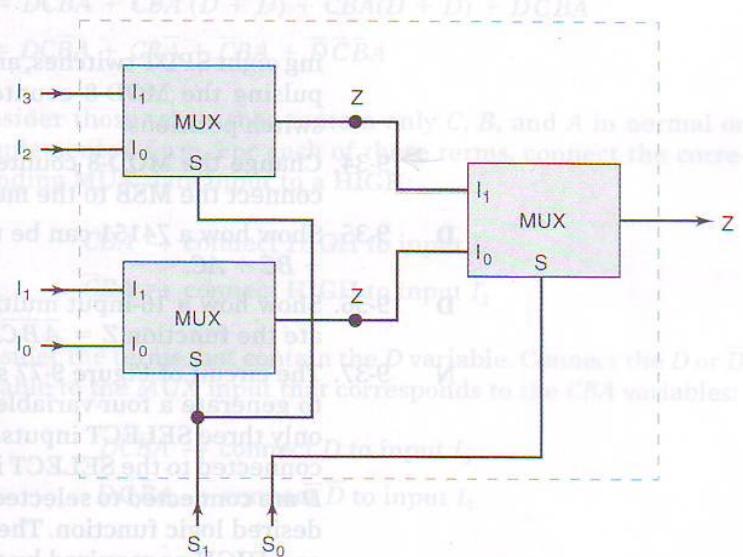

→9-29. A 4-to-1 MUX

→ 9-33. Figure 9-76 shows how a multiplexer can be used to generate logic waveforms with any desirable pattern. The pattern is programmed using eight SPDT switches, and the waveform is repetitively produced by pulsing the MOD-8 counter. Draw the waveform at Z for the given switch positions.


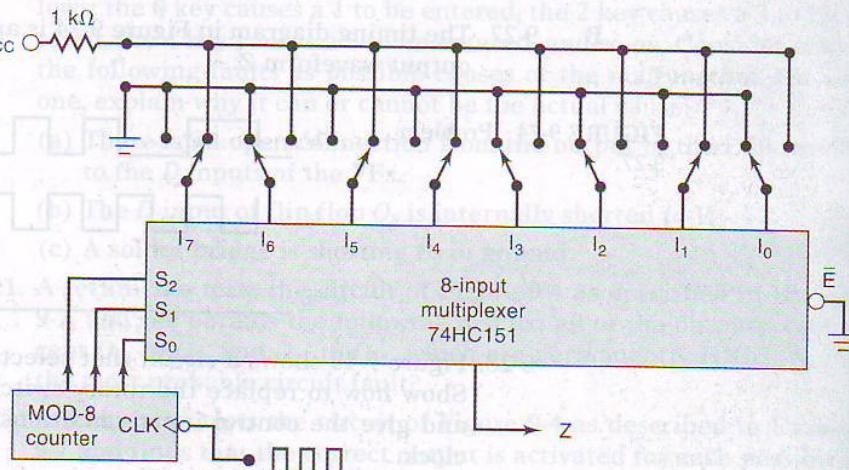


FIGURE 9-76 Problems 9-33 and 9-34.


ing eight SPDT switches, and the waveform is repetitively produced by pulsing the MOD-8 counter. Draw the waveform at Z for the given switch positions.

→ 9-33.

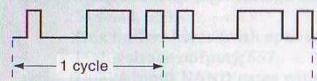


→ 9-34. Change the MOD-8 counter in Figure 9-76 to a MOD-16 counter, and connect the MSB to the multiplexer E input. Draw the Z waveform.

→ 9-34.

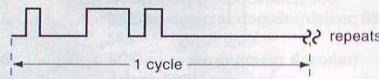

D → 9-35. Show how a 74151 can be used to generate the logic function  $Z = AB + BC + AC$ .


→ 9-35.

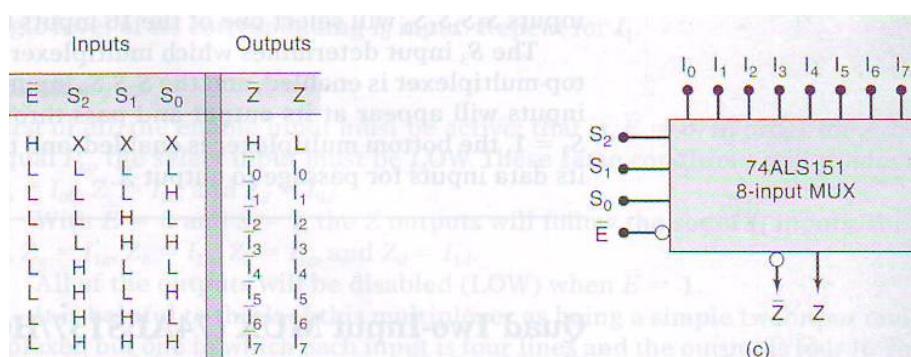

A	B	C	
0	0	0	$0 \Rightarrow I_0$
0	0	1	$0 \Rightarrow I_1$
0	1	0	$0 \Rightarrow I_2$
0	1	1	$1 \Rightarrow I_3$
<hr/>			$0 \Rightarrow I_4$
1	0	0	
1	0	1	
1	1	0	
<hr/>			$1 \Rightarrow I_6$
1	1	1	$1 \Rightarrow I_7$

N → 9-37. The circuit of Figure 9-77 shows how an eight-input MUX can be used to generate a four-variable logic function, even though the MUX has only three SELECT inputs. Three of the logic variables A, B, and C are connected to the SELECT inputs. The fourth variable D and its inverse  $\bar{D}$  are connected to selected data inputs of the MUX as required by the desired logic function. The other MUX data inputs are tied to a LOW or a HIGH as required by the function.

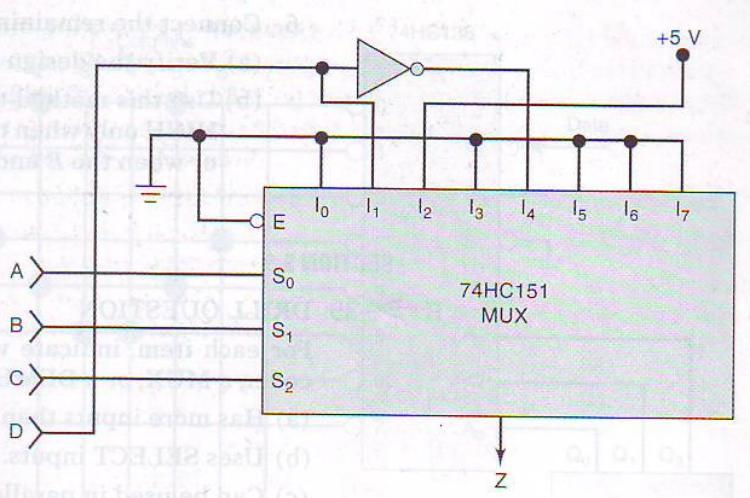- (a) Set up a truth table showing the output Z for the 16 possible combinations of input variables.



- (b) Write the sum-of-products expression for Z and simplify it to verify that

$$Z = \bar{C}B\bar{A} + D\bar{C}\bar{B}A + \bar{D}C\bar{B}\bar{A}$$

→ 9-37. Z = HIGH for DCBA = 0010, 0100, 1001, 1010.

### → 9-39. DRILL QUESTION

For each item, indicate whether it is referring to a decoder, an encoder, a MUX, or a DEMUX.

- (a) Has more inputs than outputs.
- (b) Uses SELECT inputs.
- (c) Can be used in parallel-to-serial conversion.
- (d) Produces a binary code at its output.
- (e) Only one of its outputs can be active at one time.
- (f) Can be used to route an input signal to one of several possible outputs.
- (g) Can be used to generate arbitrary logic functions.

→ 9-39. (a) Encoder, MUX (b) MUX, DEMUX  
 (c) MUX (d) Encoder (e) Decoder, DEMUX  
 (f) DEMUX (g) MUX